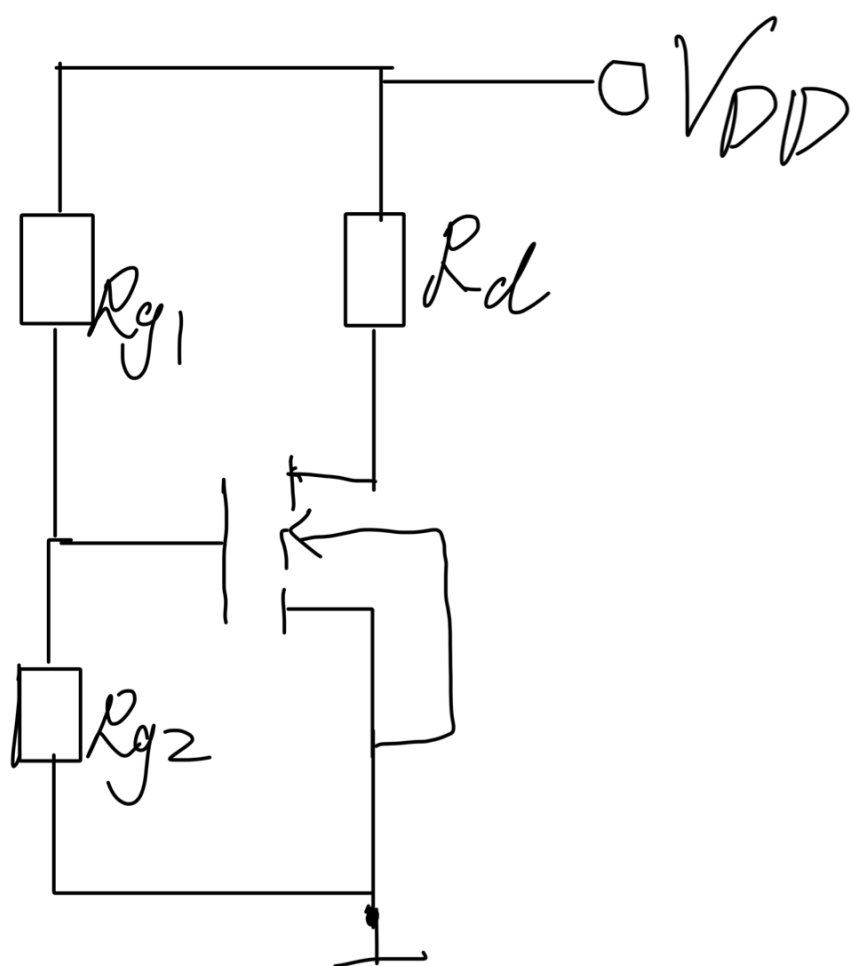




$$V_G = \frac{R_{g2}}{R_{g1} + R_{g2}} V_{DD} = 2V$$

$$V_S = 0V$$

$$V_{GS} = V_G - V_S = 2V$$

$$I_D = K (V_{GS} - V_{th})^2 = 0.8mA$$

$$V_{DS} = V_{DD} - I_D R_d = 3.4V$$

$$V_{DS} > V_{GS} - V_{th} = 1V, \text{ 位于饱和区}$$